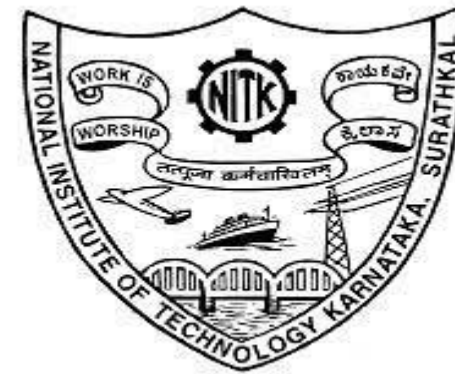


B. Tech. 3rd Semester
Design of Digital Systems (CS201)

Mini project final report on BLOOD COMPATABILITY

➤ Team members:

- Tejus V S 211CS159 ,mobile no.9113062535
- Gowtham A H 211CS124,mobile no.7795381545



DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING
NATIONAL INSTITUTE OF TECHNOLOGY KARNATAKA
SURATHKAL

➤ ABSTRACT:

A **blood bank** is a center where blood gathered as a result of blood donation is stored and preserved for later use in blood transfusion.

More likely blood transfusions mistakes occur when incorrect blood is given to a patient ,and it can have catastrophic consequence

- **Donor and patient's blood should be compatible for blood transfusion. so the purpose of this project is to design a circuit to check compatibility for transfusion.**
- **With the help of circuit using logic gates, we detect the possibilities of bloods which donor can give to, and among the possibilities if the patient's blood is matched then we can make transfusion.**
- **And also the donor should not have infections such as syphilis etc.**
- **And depending upon the amount of blood loss, priority is given to a patient and chosen for efficiency without any bias towards a patient**

➤ Introduction

Significance of Blood compatibility

A blood bank is a center where blood gathered as a result of blood donation is stored and preserved for later use in blood transfusion. More likely blood transfusions mistakes occur when incorrect blood is given to a patient ,and it can have catastrophic consequence

- Donor and patient's blood should be compatible for blood transfusion. so the purpose of this project is to design a circuit to check compatibility for transfusion.
- With the help of circuit using logic gates, we detect the possibilities of bloods which donor can give to, and among the possibilities if the patient's blood is matched then we can make transfusion.
- And also the donor should not have infections such as syphilis etc.

TYPE	YOU CAN GIVE BLOOD TO	YOU CAN RECEIVE BLOOD FROM
A+	A+, AB+	A+, A-, O+, O-
O+	O+, A+, B+, AB+	O+, O-
B+	B+, AB+	B+, B-, O+, O-
AB+	AB+	EVERYONE
A-	A+, A-, AB+, AB-	A-, O-
O-	EVERYONE	O-
B-	B+, B-, AB+, AB-	B-, O-
AB-	AB+, AB-	AB-, A-, B-, O-

Fig 1: chart table of blood compatibility

- From the figure shown , it is clear that , we can't transfer blood to any person without compatible test. a person of random blood group can't receive/donate to everyone .
- From the figure we can see that O- is universal donor and AB+ is universal receiver.
- Blood group can be determined by 3 factors, human can have 2 antigens in RBC , A,B depending on their presence and also rh factor if it is present it is positive else negative . Determines a blood group.

➤ TRUTH TABLE

Ad	Bd	Ap	Bp	Op	ABp
0	0	1	1	1	1
0	1	0	1	0	1
1	0	1	0	0	1
1	1	0	0	0	1

Rh (+/-)	+p	-p
1	1	0
0	1	1

➤ in truth table you can see that Ad and Bd are antigens present in donor are the inputs, and Ap,Bp,Op,ABp represents blood groups of patients if it's 1 he can receive if 0 can't. are outputs .

➤ Rh (+/-) is also a factor in donor is an input and +p,-p are rh factors of patient are output.

➤ Boolean expression

- $Ap = \sim Bd$
- $Bp = \sim Ad$
- $Op = \sim (Ad + Bd) = \sim Ad \sim Bd$
- $Abp = 1$
- $+p = 1$
- $-p = \sim Rh$

Most Common Blood Group in India

Here is the average blood type distribution in the Indian population:

- O+ = 32.53%
- O- = 2.03%
- A+ = 21.8%
- A- = 1.36%
- B+ = 32.09%
- B- = 2.01%
- AB+ = 7.70%
- AB- = 0.48%

Therefore we see that the **most common blood group in India is O positive**. The second most prevalent blood group in India is B positive. **AB negative is the rarest blood group in India**.

Fig 2 : distribution of blood group in india


Ex: suppose there is a donor of AB- and 2 patient of AB- and O- , O- is selected and given blood because O- receives blood only from O- with few people having it.

➤ From the data of blood type distribution shown in the source , we can see that every blood group is not equally distributed , hence with few donors and more patients it is necessary to prioritize among patients .


➤ so priority given to patient in order

1)O- 2)B- 3)A- 4) AB-
5)O+ 6)B+ 7)A+ 8)AB+

➤ Flowchart

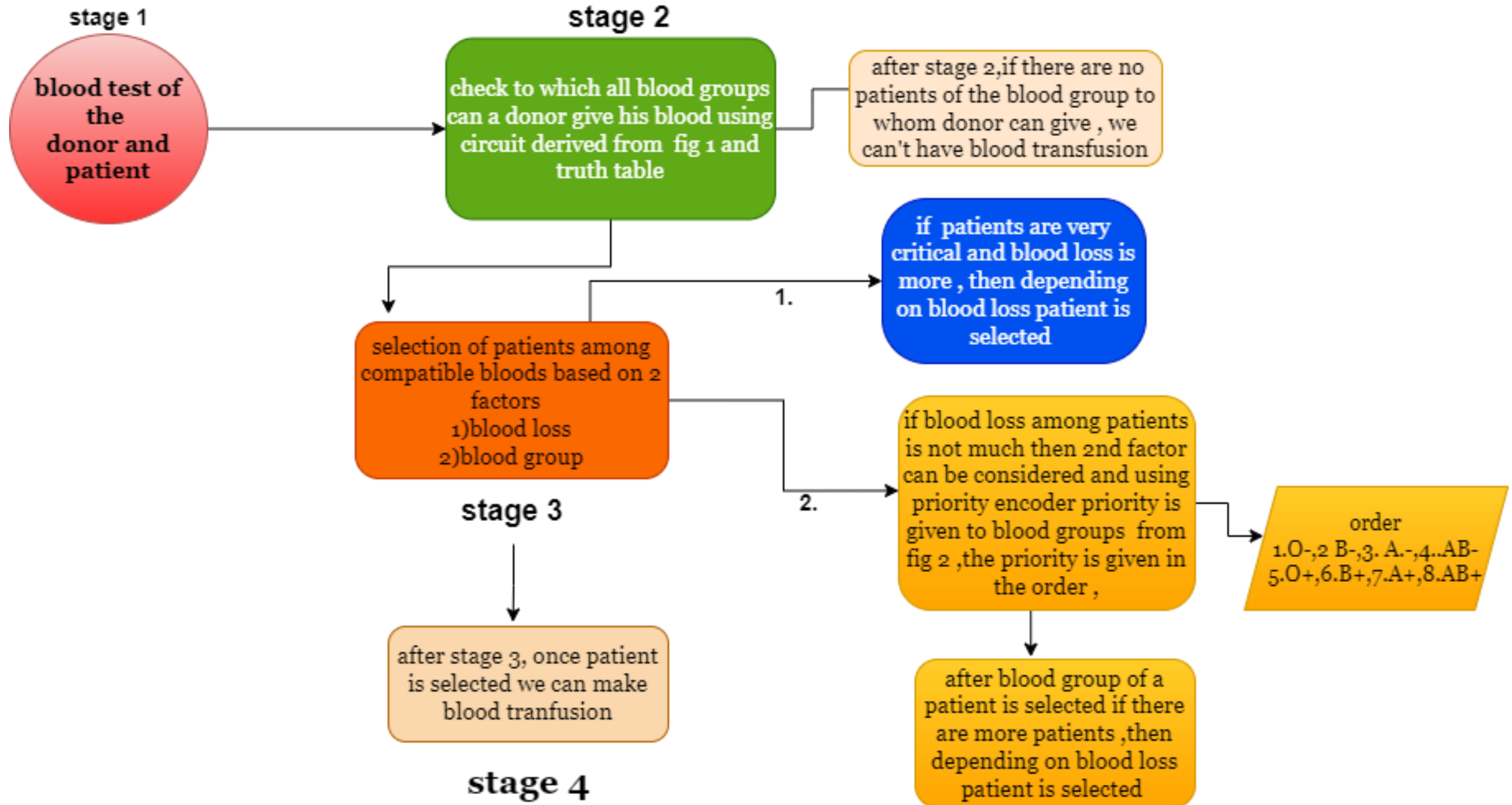

➤ Circuit diagram

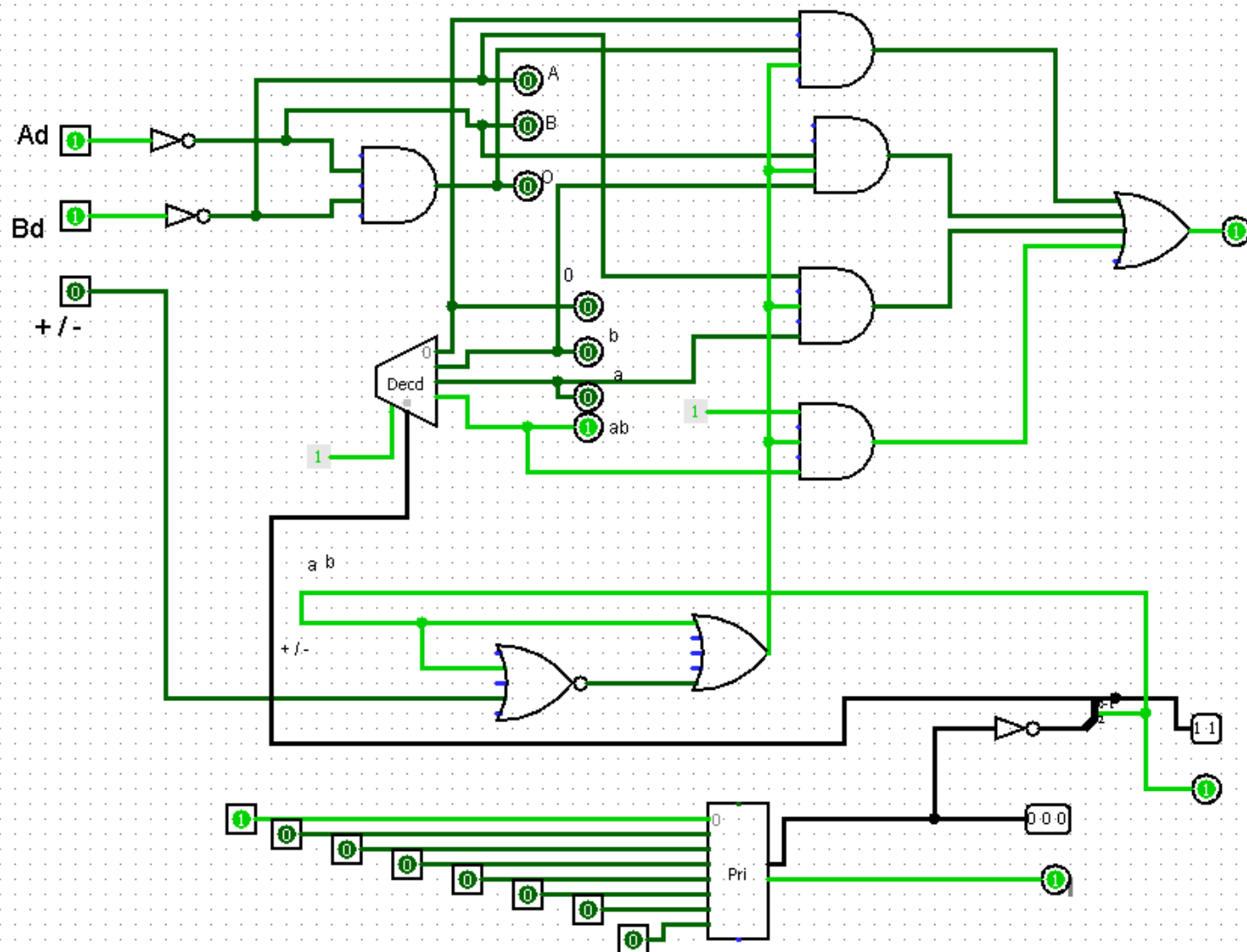

0 = AB+, 1 = A+, 2 = B+, 3 = O+, 4 = AB-, 5 = A-, 6 = B-, 7 = O-

➤ Verilog code

➤ Version 1

timescale 1ns/1ns

```
module candonate(input a ,b ,rh , output ap, bp, op,abp ,p1 ,p2
);
```

```
    assign ap=!b;
    assign bp=!a;
    assign op=!(a+b);
    assign abp=1;
    assign p1=1;
    assign p2=!rh;
```

```
endmodule
```

```
module bdec(input a,b,output ap,bp,op,abp);
```

```
    assign op=(!a)&(!b);
    assign bp=(!a)&(b);
    assign ap=(a)&(!b);
    assign abp=a&b;
```

```
endmodule
```

```
module bmatch(input
ad,bd,od,abd,rhd,ap,bp,op,abp,rhp,output x);
wire t=(!(rhd|rhp))|rhp;
assign x=t&((ad&ap)+(bd&bp)+(od&op)+(abd&abp));

endmodule
```

```
module pro;

reg a,b,rhd,a1,b1,rhp;
wire ap, bp, op,abp,p1,p2,ad,bd,od,abd,x;

candonate t1(a,b,rhd,ad,bd,od,abd,p1,p2);
bdec t2(a1,b1,ap,bp,op,abp);
bmatch t3(ad,bd,od,abd,rhd,ap,bp,op,abp,rhp,x);

initial
begin
a=0;b=0;rhd=0;a1=0;b1=0;rhp=1;
end
```

initial

begin

```
$monitor("donor:a=%d,b=%d,rhd=%d,  
patient:a1=%d,b1=%d,rhp=%d  
,compatible:x=%d",a,b,rhd,a1,b1,rhp,x);
```

end

endmodule

```
[Running] pro1.v  
donor:a=0,b=0,rhd=0, patient:a1=0,b1=0,rhp=1 ,compatible:x=1  
[Done] exit with code=0 in 0.187 seconds
```

```
[Running] pro1.v  
donor:a=1,b=0,rhd=0, patient:a1=0,b1=0,rhp=1 ,compatible:x=0  
[Done] exit with code=0 in 0.203 seconds
```

➤ Version 2:

`timescale 1ns/1ns

```
module candonate(input a ,b ,rh , output ap, bp, op,abp ,p1 ,p2 );
```

```
    assign ap=!b;
```

```
    assign bp=!a;
```

```
    assign op=!(a+b);
```

```
    assign abp=1;
```

```
    assign p1=1;
```

```
    assign p2=!rh;
```

```
endmodule
```

```
module bdec(input a,b,output ap,bp,op,abp);
```

```
    assign op=(!a)&(!b);
```

```
    assign bp=(!a)&(b);
```

```
    assign ap=(a)&(!b);
```

```
    assign abp=a&b;
```

```
endmodule
```

```
module bmatch(input
ad,bd,od,abd,rhd,ap,bp,op,abp,rhp,output x);
wire t=(!(rhd|rhp))|rhp;
assign x=t&((ad&ap)+(bd&bp)+(od&op)+(abd&abp));
```

```
endmodule
```

```
module bprio(input d0,d1,d2,d3,d4,d5,d6,d7,output x,y,z);
```

```
assign x=!(d7|d6|d5|d4);
```

```
assign
```

```
y=!( (((!(d7|d6|d5|d4|d3))&d2)|((!(d7|d6|d5|d4))&d3)|d7|d6)
```

```
;
```

```
assign
```

```
z=!(d7|(((!(d7|d6))&d5)|((!(d7|d6|d5|d4))&d3)|((!(d7|d6|d5|
d4|d3|d2))&d1)));
```

```
endmodule
```

```
module pro;
```

```
reg a,b,rhd,d0,d1,d2,d3,d4,d5,d6,d7;
```

```
wire ap, bp, op,abp,p1,p2,ad,bd,od,abd,x,rhp,a1,b1;
```

```
bprio test(d0,d1,d2,d3,d4,d5,d6,d7,rhp,a1,b1);
```

```
candonate t1(a,b,rhd,ad,bd,od,abd,p1,p2);
```

```
bdec t2(a1,b1,ap,bp,op,abp);
```

```
bmatch t3(ad,bd,od,abd,rhd,ap,bp,op,abp,rhp,x);
```

```
initial
```

```
begin
```

```
    d0=0;d1=0;d2=0;d3=0;d4=0;d5=0;d6=0;d7=1;a=0;b=0;rhd=0;
```

```
end
```

```
initial
```

```
begin
```

```
$monitor("donor:a=%d,b=%d,rhd=%d,
```

```
patients:d0=%d,d1=%d,d2=%d,d3=%d,d4=%d,d5=%d,d6=%d,d7
```

```
=%d ,compatible:x=%d",a,b,rhd,d0,d1,d2,d3,d4,d5,d6,d7,x);
```

```
end
```

output

PROBLEMS OUTPUT DEBUG CONSOLE TERMINAL

[Running] pro2.v

donor:a=0,b=0,rhd=0, patients:d0=0,d1=0,d2=0,d3=0,d4=0,d5=0,d6=0,d7=1 ,compatible:x=1

[Done] exit with code=0 in 0.973 seconds

[Running] pro2.v

donor:a=1,b=0,rhd=0, patients:d0=0,d1=0,d2=0,d3=0,d4=0,d5=0,d6=0,d7=1 ,compatible:x=0

[Done] exit with code=0 in 0.546 seconds

[Running] pro2.v

donor:a=0,b=0,rhd=0, patients:d0=0,d1=0,d2=0,d3=0,d4=0,d5=0,d6=1,d7=0 ,compatible:x=1

[Done] exit with code=0 in 0.463 seconds

➤ Conclusions and future work

- the circuit can be used in blood banks in order to verify the blood compatibility between the donor and patient blood, and can avoid incorrect transfusions which leads to catastrophic consequences.
- it can increase the efficiency in blood banks , can choose the critical patients and serve them first without any bias .
- this circuit can be linked to blood test machine where the output of the machine can be given as input to the the circuit and can give us quick results .
- the circuit may be simple but crucial and beneficial.

➤ References:

- Digital design morris mano.
- [Blood Type Compatibility | Memorial Blood Centers \(mbc.org\)](http://www.mbc.org)
- [Blood compatibility testing - Wikipedia](https://en.wikipedia.org/wiki/Blood_compatibility_testing)